

O3: Sensors, Actuators, and I/O

Reminders:

- Labs start today/tomorrow!
Please install the Arduino IDE ahead of time and bring supplies/micro USB cable if you have them
- No late prelabs





Homeworks

- ◆ Due before class Wednesday and Friday
- ◆ First one is out at the end of class
- ◆ Smaller, theoretical assignments
 - ◇ Typically a short reading and 1-3 questions
- ◆ Graded on **good-effort completion**
 - ◇ A preview of material taught in lecture
 - ◇ You're not expected to know it perfectly
 - ◇ If you get stuck, write down why you're stuck and move on



Community guidelines

- ◆ Do not assume what people do/do not know
- ◆ Treat everyone with respect
 - ◇ Trust intent, acknowledge impact
- ◆ Give space to ask/answer questions
- ◆ Active listening
- ◆ Teamwork over competition



Review

- ◆ Circuits are loops through which electricity flows (have a power source and some conductors)
- ◆ We learned computations for voltage, current, and power




Interpreting device data sheets

- Often, we assume:
 - Wires are perfect conductors
 - Constant resistance
 - Constant forward voltage
 - Discrete (on/off) or at least linear behavior
- In reality: interference; variations with supply voltage, temperature, etc

[Yellow LED data sheet](#)

What is the actual minimum resistance?

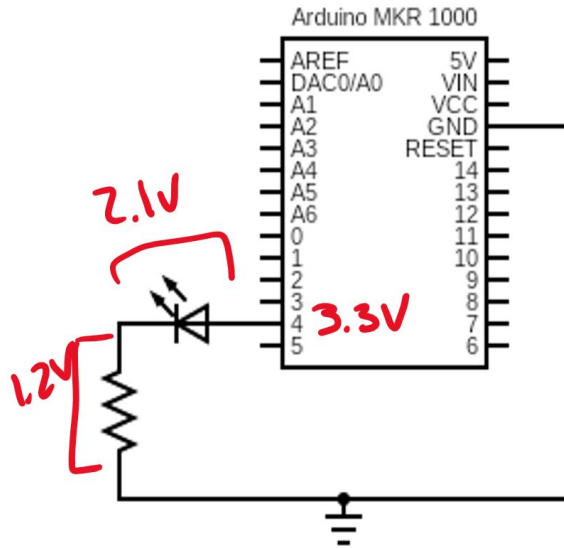


$$\leq 7 \text{ mA}$$

$$V = IR$$

$$1.2\text{V} = (7\text{mA}) \cdot R$$

$$R \geq \frac{1.2\text{V}}{7\text{mA}}$$



So are we stuck deciphering datasheets all day?

No: make reasonable assumptions to get a tolerance in safe values



Digital devices


Leds are digital **output** devices

Things like push buttons are digital **input** devices

(**When connected correctly**) are driven by or produce a high/low signal



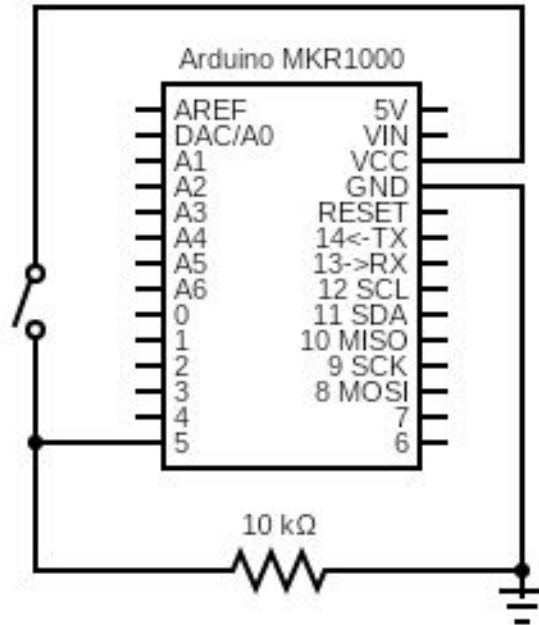
Circuit principle: must be closed for electricity to flow



Input components


Your book talks about:

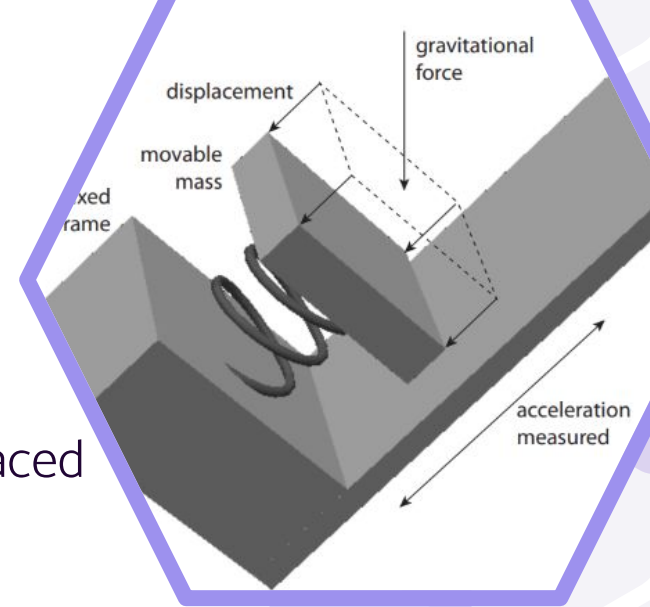- Accelerometers (measure acceleration of displaced mass)
- Anemometers (air flow for velocity)
- GPS (satellite for position)
- Gyroscopes (gimbals and modern)
- Microphones
- Engine controllers, thermometers, cameras, chemical sensors, etc



Other input components in your kits

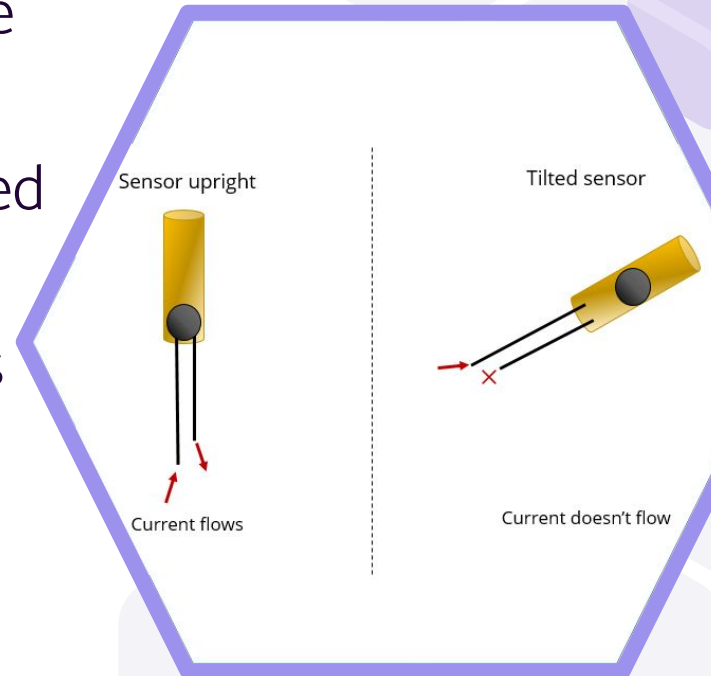- ◆ Thermistor/Photoresistor - resistance changes based on temperature/light
- ◆ Potentiometer - divides voltage* based on rotation of the dial
- ◆ Tilt sensor - Metal bearing completes circuit




Output components

Your book talks about:

- LEDs
- Motors (DC)

Your kits have:

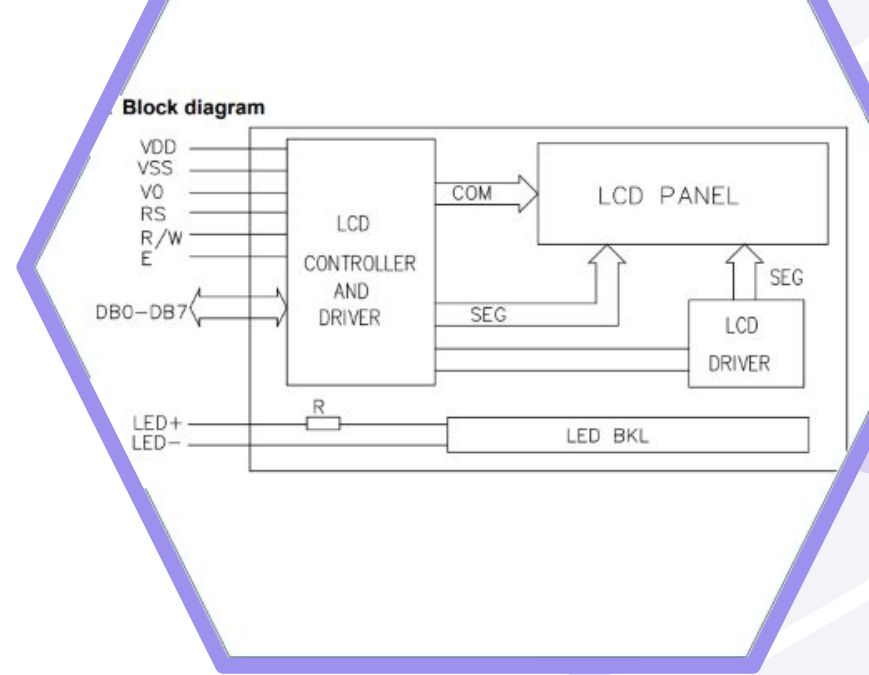- LCD screen (controlled digitally)
- Servo motor (controlled by lengths of high/low pulses)
- Piezo speaker (electricity displaces film to make sound)



[Image source](#)





*How do you control a device
that has higher
power/voltage/current
requirements than your
Arduino can provide?*

Transistors

Basically an electric switch

Voltage applied to **G**ate connects **D**rain and **S**ource

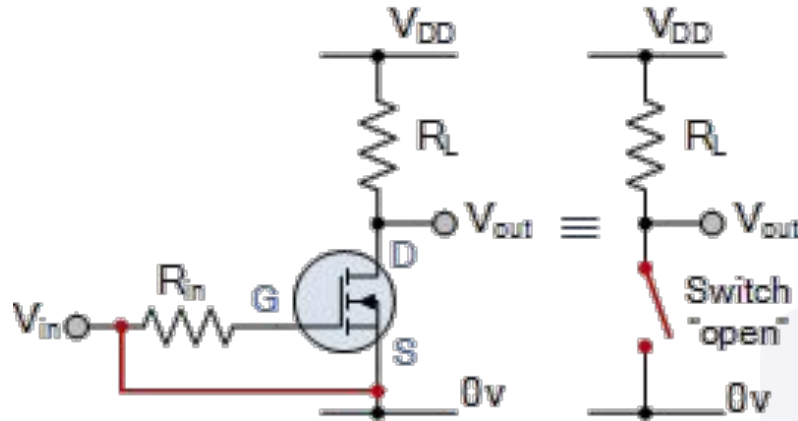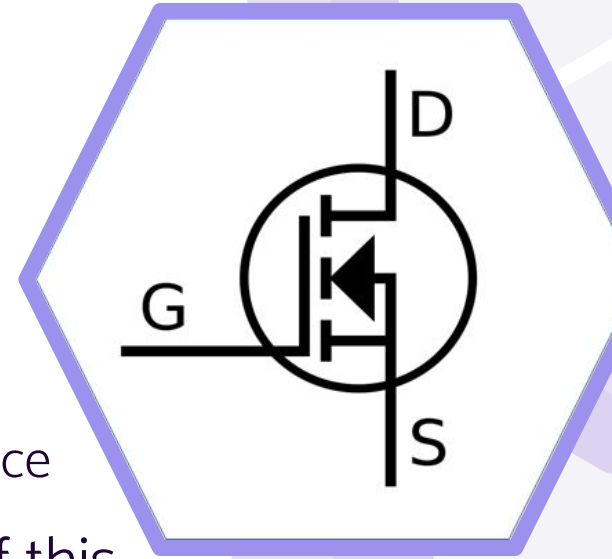
Come in different types (beyond the scope of this course)



Be careful when using transistors!

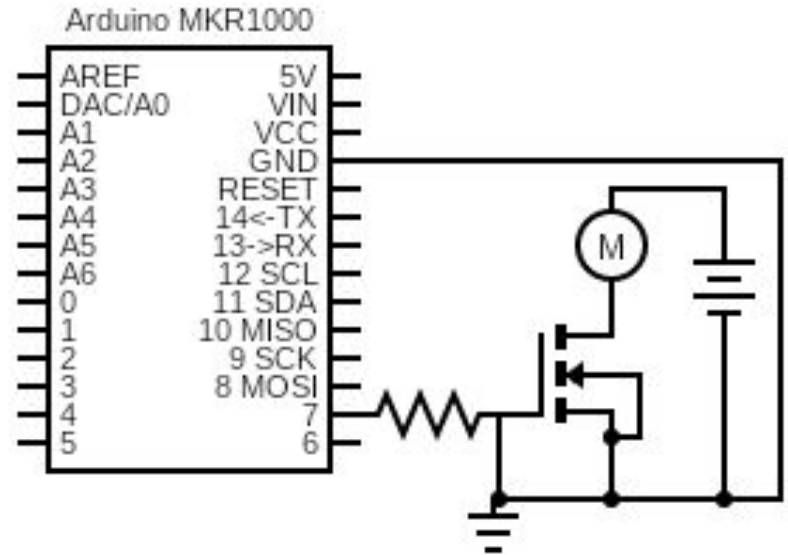
Problems with this circuit:

- Issues with [FET in kit](#):
 - Gate voltage
 - Current
- No isolation between Arduino and higher-voltage circuit



Optocouplers

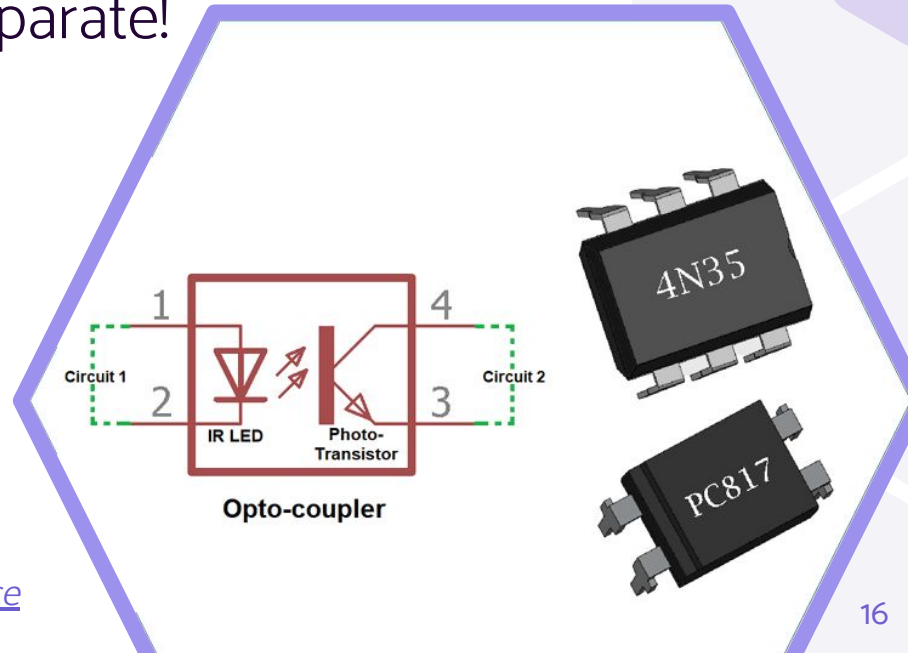- Control one circuit using another, but they are completely electrically separate!



[Image source](#)

A better circuit

Still need to
double-check
datasheets!

